



Fully digital Class-D amplifiers

by using a multibit sigma-delta converter (noise-shaper)

<https://github.com/YetAnotherElectronicsChannel>

<https://www.youtube.com/c/YetAnotherElectronicsChannel>

Audio PWM modulation theory

 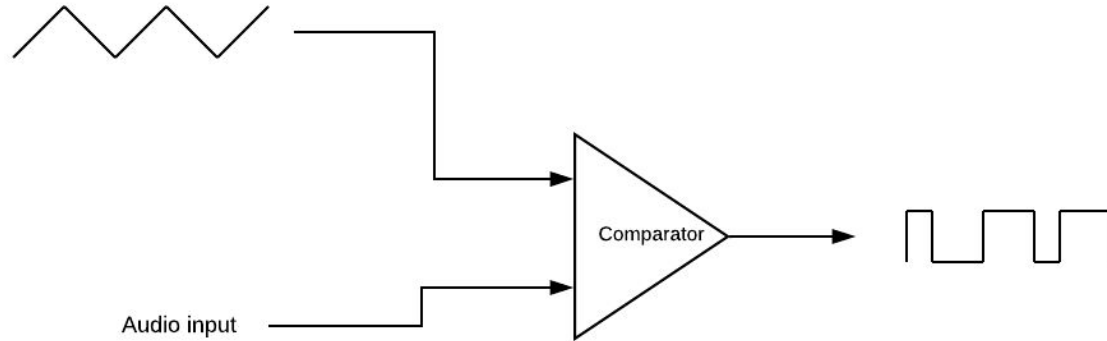


Picture from:

<https://www.fairaudio.de/lexikon/puls-weiten-modulation/>

Audio PWM modulation theory - digital

 - Overall concept stays the same
- Drawback: Triangle waveform is implemented as running counter
no perfect triangle waveform



Audio PWM modulation theory - digital

- PWM frequency needed for Class-D power-stage (~ 200-500 kHz)
- For good audio quality : PWM-resolution needed ≥ 16 bits
- Triangle-generator (counter) must run with every PWM period one time up and one time down ($2 * 2^{16}$ steps = 131072 clock-cycles needed for one period)
- For 200 kHz switching frequency, the digital clock-frequency needed is $200000 * 131072 = \underline{\underline{26.2 \text{ GHz}}}$
- 26.2 GHz is impossible to realize on a low-cost FPGA (50 - 100 MHz)

Audio PWM modulation theory - digital

Assuming a 100 MHz clock on FPGA modulating a 200 kHz PWM

-> $100\text{MHz} / 200\text{kHz} = 500$ clock cycles available for each PWM period

-> Counter must run one time up and down with 500 clock-cycles -> resolution is ~ 250 steps (approximately 8 Bit)

-> 8 Bit is a very bad audio quality

Example digital Class-D (TI TAS5701)

- Full digital Class-D amplifier with I²S input
- TI most probably uses a mixed power / digital technology to combine power mosfets and digital logic on the same silicon die
- **Drawback:** Those technologies can run digital logic comparable to a low-cost FPGA (100 to max. 150 MHz) -> how is it possible to achieve a good audio quality?



TAS5701

www.ti.com

SLOS559A – JUNE 2008 – REVISED AUGUST 2010


20-W STEREO DIGITAL AUDIO POWER AMPLIFIER

Check for Samples: [TAS5701](#)

Example digital Class-D (TI TAS5701)


- Audio chain contains a “SRC” -> Sample-Rate Converter
- Audio chain contains a “4th order Noise Shaper and PWM”
- How is it working in detail? -> Let's implement it on a FPGA!

FUNCTIONAL BLOCK DIAGRAM

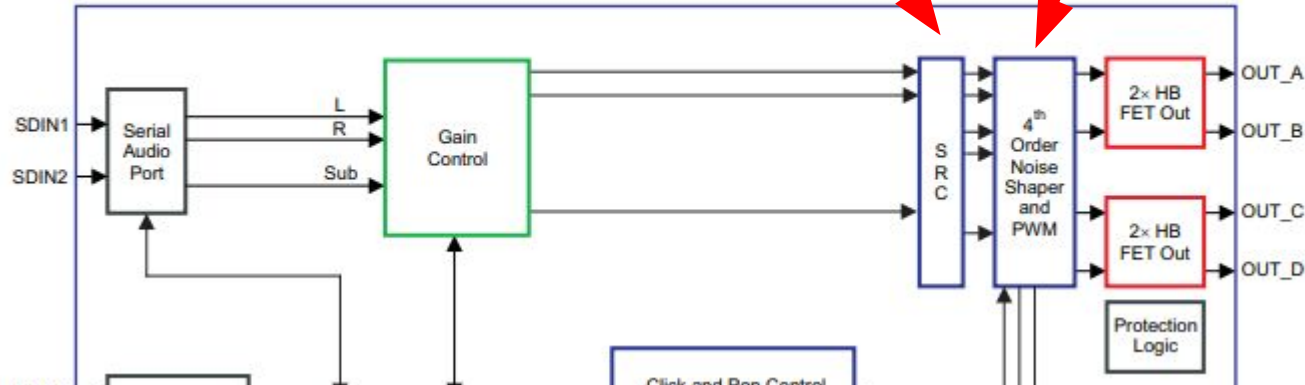


Introduction - Sigma Delta Conversion

- Sigma Delta converts an analog signal into a 1-bit bitstream (same signal represented in 1's and 0's)
- Output bitstream is based on a clock
- The output signal is **ideally** the same as the input signal
- Practically the signal quality depends on the “oversampling rate” (baseband-frequency of the signal vs clocking speed of the modulator) -> the more oversampling, the better the output signal regarding signal-noise ratio

 


Introduction - Sigma Delta Conversion


- Reducing the resolution of a signal (bit-width) is introducing “quantization noise” (also in the baseband of the signal)
- A sigma-delta converter is shifting or “shaping” the quantization-noise in the baseband signal into higher-frequency ranges if the signal is oversampled -> therefore called “noise-shaper”
- As the noise is shifted out of the baseband-signal, it’s not hearable anymore for humans

 

Baseband signal

 


Baseband signal (oversampled)

 


Baseband signal
(oversampled + "noise shaped")

Multibit Sigma-Delta / Noiseshaper

- The output-comparator (only 1 bit resolution) of the sigma-delta converter is replaced now by a x-Bit “quantizer”
- The output data-width is reduced from 24-bit to e.g. 4 bits
- Signal quality on the output ideally the same as on the input (depends on oversampling-ratio)
- Multiple integrators can be connected in series, reducing the amount of oversampling for the same signal quality (TI TAS5701 example = 4th order = 4 integrators)

 

High-res audio PWM modulation

 

- The 96 kHz audio signal is converted to $f_s=384$ kHz with a SRC
- The noise-shaper reduces the bit-width of the audio-signal from 24 bit to 5 bit (with almost the same audio quality as on the input)
- Oversampling ratio is $= 384 \text{ kHz} / (2 * f_{\text{baseband}} \sim 40 \text{ kHz}) = 9,6 \sim 10$
- PWM modulator needs $(2 * 2^5 * 384 \text{ k clock cycles}) = 24,576 \text{ MHz}$
- **24,6 MHz is realizable on a cheap FPGA or mixed-signal silicon technology :-)**

High-res audio PWM modulation


Remember: This is only an example how I implemented it

- Improving audio quality is possible by e.g. running the clock with 4×24.6 MHz and using a 7 Bit PWM modulator instead
- But the iCE 40 FPGA on my TinyFPGA-BX board is not really capable of running higher than approx. 40 MHz for math-operations with > 24 bit values (improvements with more expensive FPGAs possible)
- My humble information I have about the TI device is, that it even works internally with an 8-Bit PWM (not confirmed 100%)


Image from:

<https://forums.cockos.com/showthread.php?t=215201>

Upsampling (SRC)

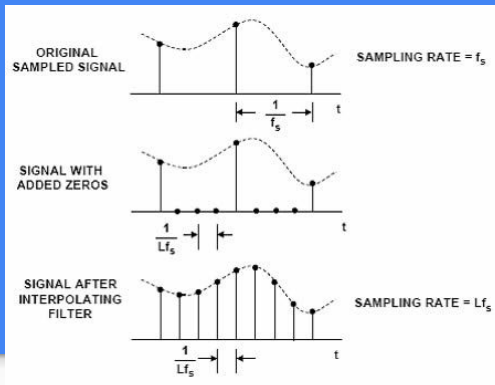

 
- Between every incoming sample, 3 zero-samples are introduced and finally low-pass filtered by a FIR filter with cut-frequency at ~ 20 kHz
- This process reduces the signal-energy by the upsampling-factor (4)
- Incoming samples must be multiplied by 4 before to keep the same audio-level at the output



Upsampling (SRC)

- In my implementation, the FIR filter has 124 coefficients, but as 75% of all samples are 0, the zero-samples must not be processed actually
- => effectively $124/4 = 31$ multiplication- and summing operations per incoming sample needed (with a 24,6 MHz clock, there are 64 clock-cycles available for each of the incoming 384 kHz samples)

4th order Noise Shaper (CIFB structure)

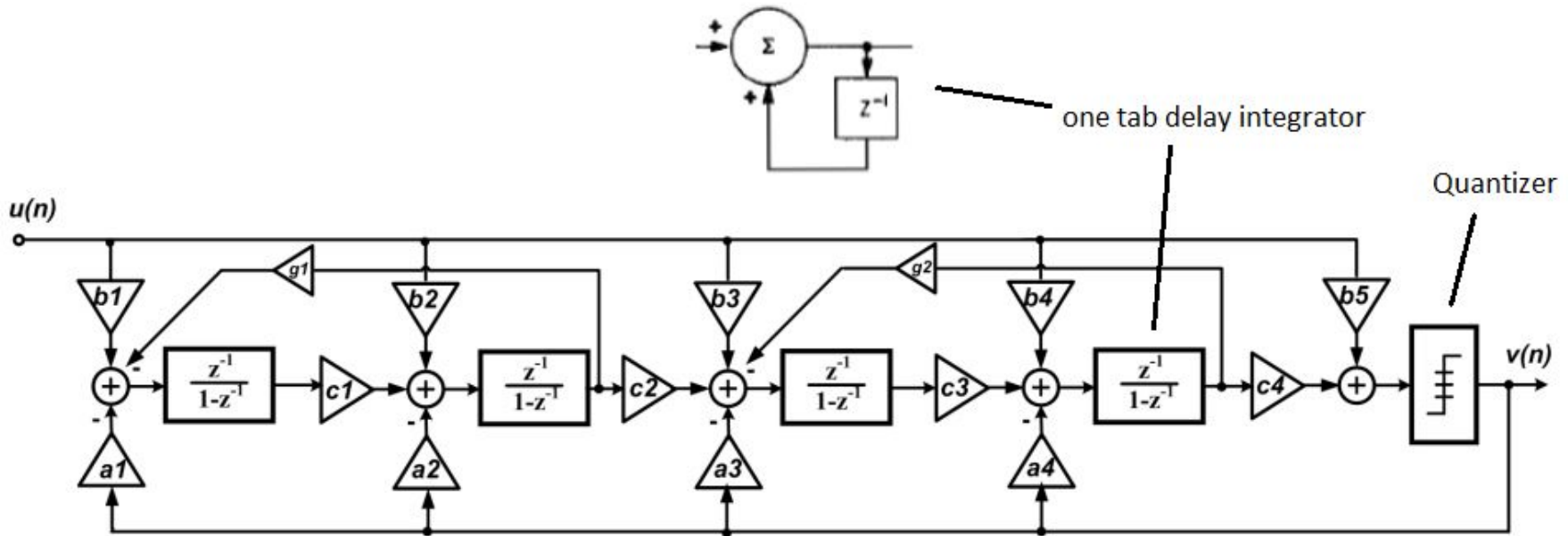


Parameter c is always 1

4th order Noise Shaper

- Calculation of all parameters (b_1 - b_5 , a_1 - a_4 , g_1 , g_2) is very critical to obtain optimal signal/noise performance and being stable
- Tools / Documentation available for determining the parameter-set
 - Matlab Delta-Sigma Toolbox ([Link](#))
 - Delta-Sigma Toolbox by University of Ulm ([Link](#))
 - Application Notes on the Web ([Link](#))
- In my FPGA example, I even hand-adjusted the parameters of the g_1 and g_2 resonators for improving audio-quality
- I wasn't lucky with the Matlab-tool / tool from University of Ulm
 - Parameter-set of University of Ulm was always unstable (distorted noise on the output)
 - Parameter-set of Matlab-tool was stable, but signal/noise performance was terrible
 - I used the parameter-set of the app-note above for b_1 - b_5 and a_1 - a_4 ... g_1 + g_2 I was adjusting "by hand" via a SPI interface in the FPGA for manipulating the parameters in realtime (not present anymore in my published GitHub project now)

Actual FPGA implementation

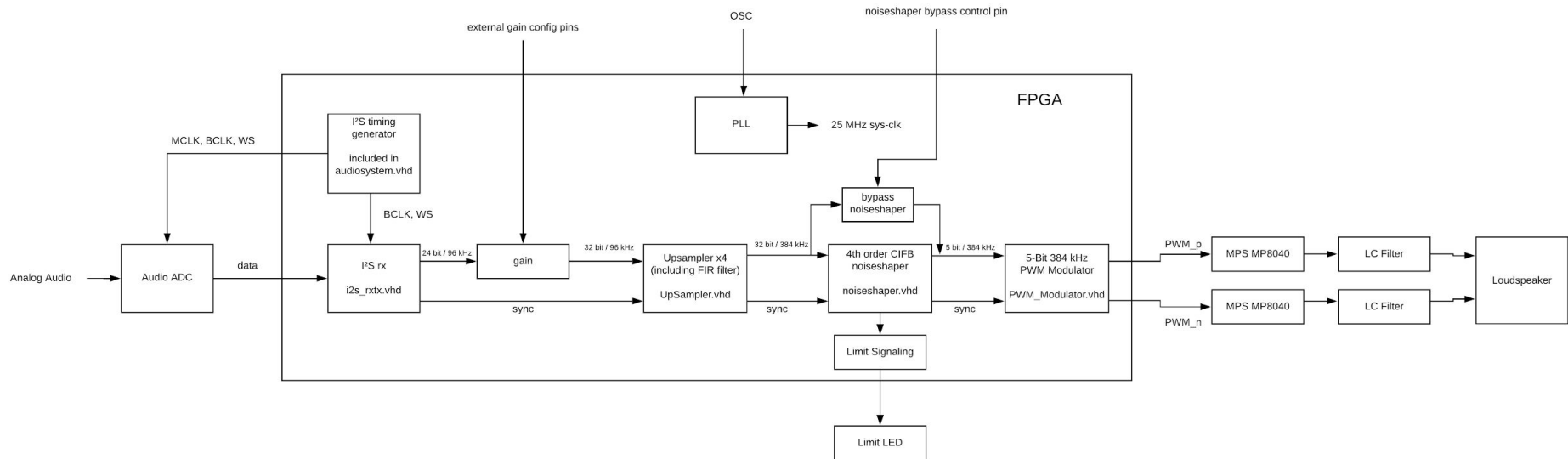

Real clocking &
frequencies:

$MCLK = 25 \text{ MHz} / 2 = 12.5 \text{ MHz}$
 $BCLK = 25 \text{ MHz} / 4 = 6.25 \text{ MHz}$
 $WS = 25 \text{ MHz} / 256 = 97.6 \text{ kHz}$
 $PWM = 25 \text{ MHz} / 64 = 390 \text{ kHz}$

Implementation hints

- Your system **MUST** run fully synchronous
 - E.g. the 64 counter steps of the PWM modulator must be in sync with the 384 kHz audio-stream from the noise-shaper
 - Therefore not implementable on a μC (e.g. STM32)
- Upsampling by a factor power-of-2 is easy to implement because of multiplication of power-of-2 by just bit-shifting to the left
- PWM frequency is therefore also a power-of-2 multiple of the input sample rate (check out switching frequency of the TI TAS5701 device)

PWM OPERATION AT RECOMMENDED OPERATING CONDITIONS

PARAMETER	TEST CONDITIONS	MODE	VALUE	UNIT
Output sample rate $2\times$ – $1\times$ oversampled	32-kHz data rate $\pm 2\%$	$12\times$ sample rate	384	kHz
	44.1-, 88.2-, 176.4-kHz data rate $\pm 2\%$	$8\times$, $4\times$, and $2\times$ sample rates	352.8	kHz
	48-, 96-, 192-kHz data rate $\pm 2\%$	$8\times$, $4\times$, and $2\times$ sample rates	384	kHz

Implementation hints

- I used fixed-point arithmetic for all math-operations on the FPGA
- Check out my video about IIR filters on FPGA where I explained how fixed-point arithmetic on a FPGA is working

<https://www.youtube.com/watch?v=eE6Qwv997cs>

<https://github.com/YetAnotherElectronicsChannel/FPGA-Audio-IIR>